
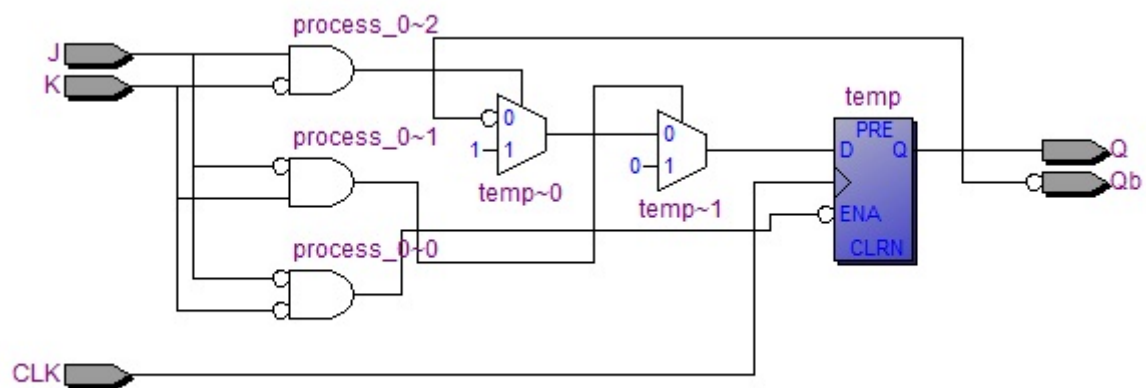



RTL Diagram for J-K Flip Flop:

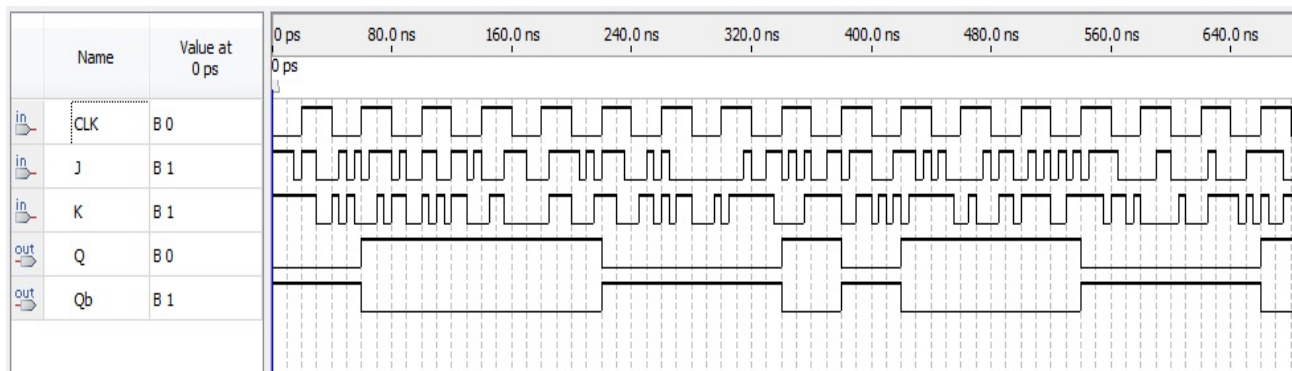


Output Waveform for J-K Flip Flop:




RTL Diagram for S-R Flip Flop:

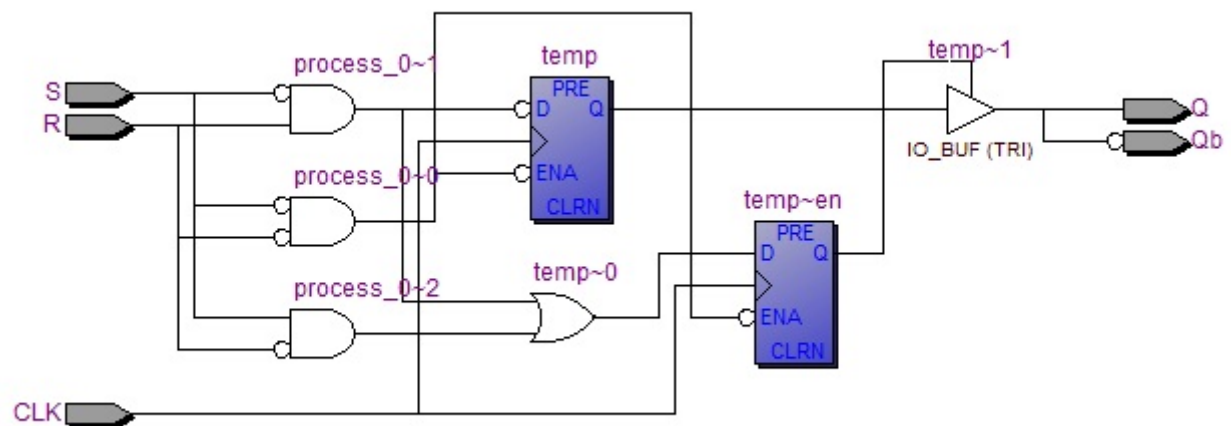


Output Waveform for S-R Flip Flop:

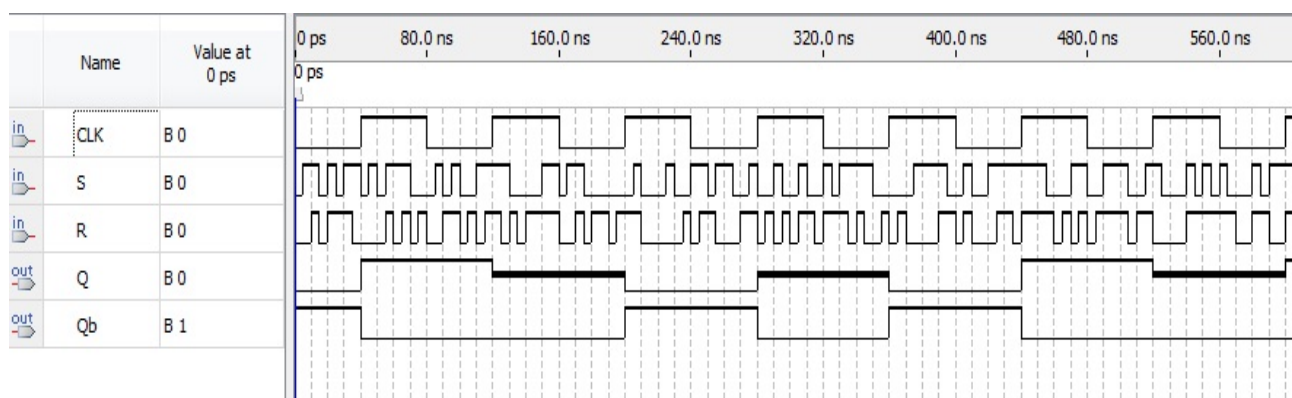

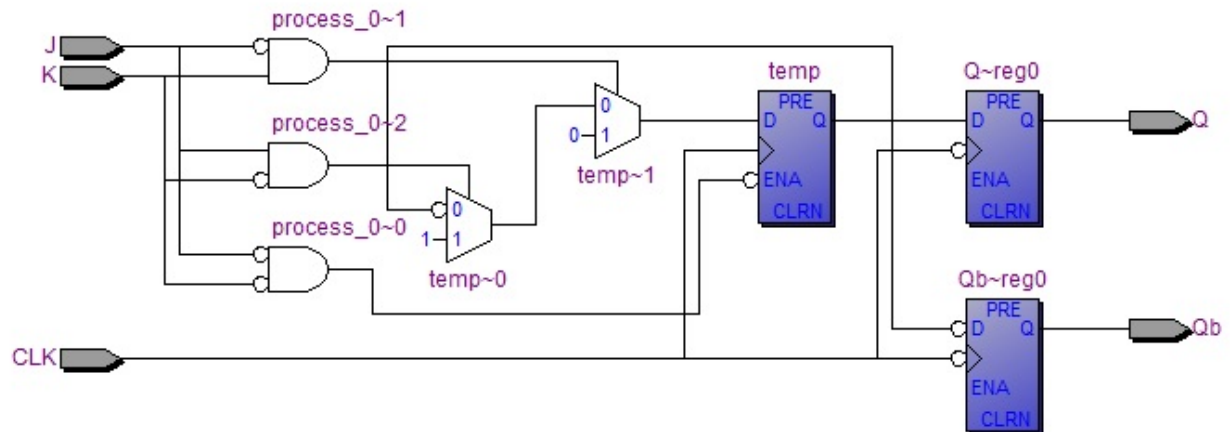
RTL Diagram for J-K Master Slave Flip Flop:



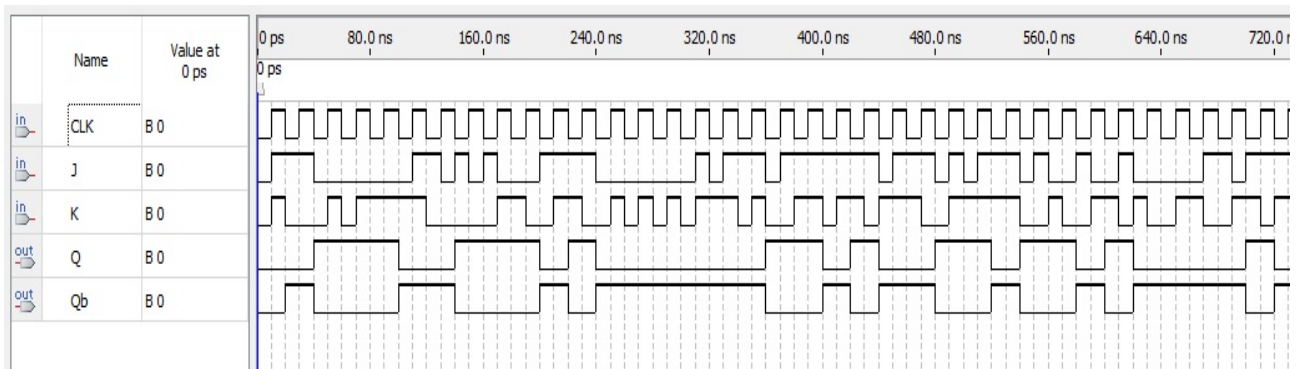Output Waveform for J-K Master Slave Flip Flop:



RTL Diagram for D Flip Flop:

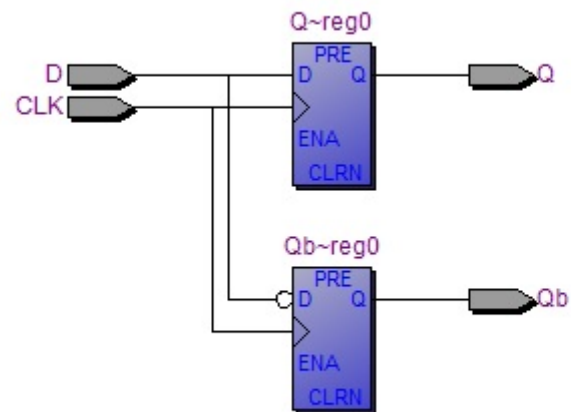

Output Waveform for D Flip Flop:

