RTL Diagram for 3:8 Decoder
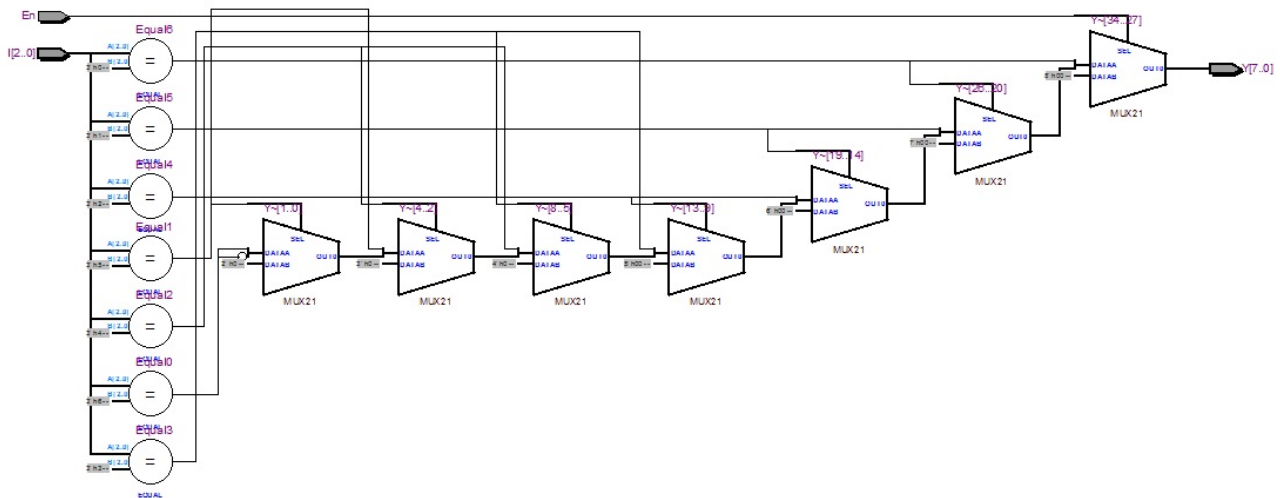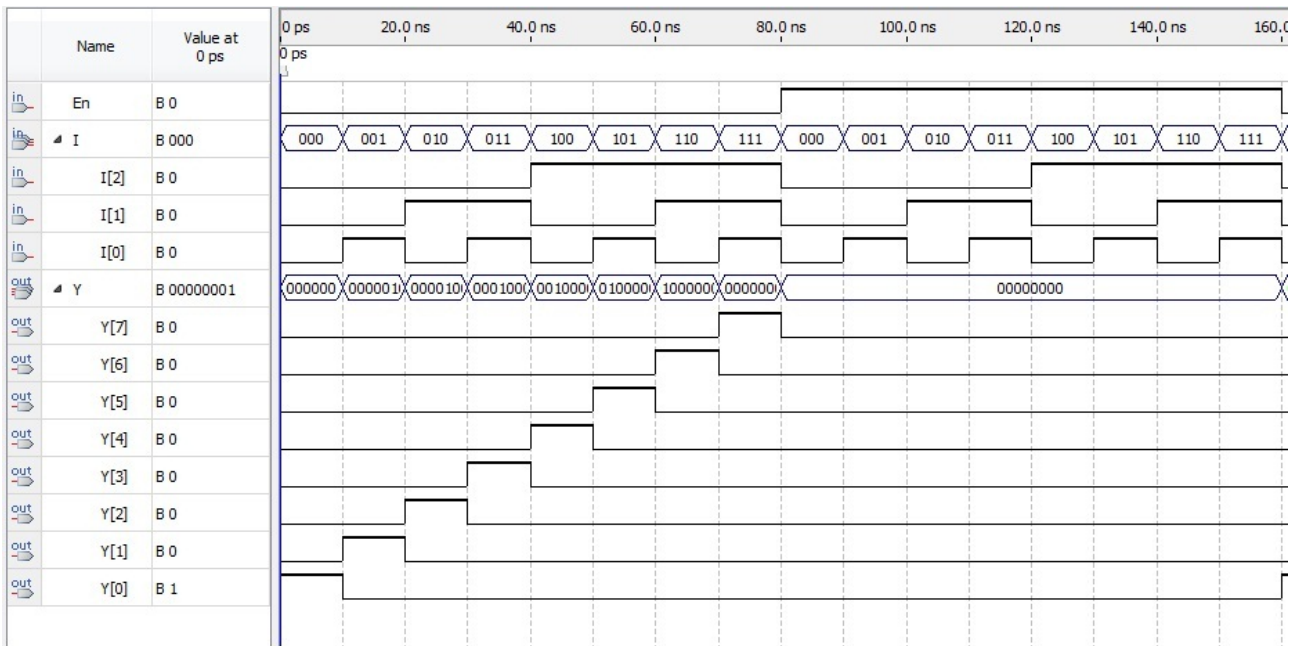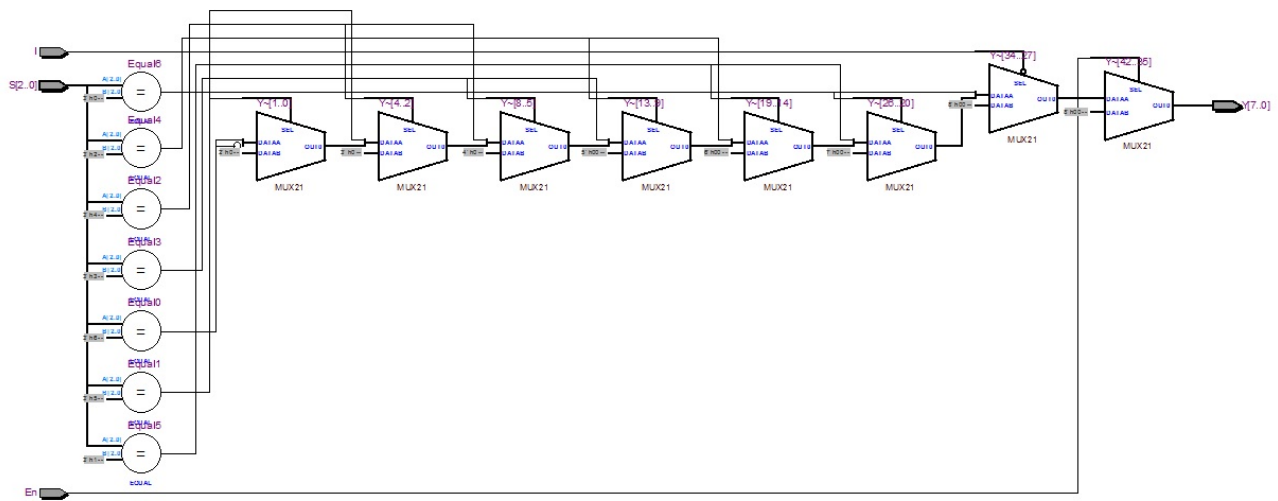

Output Waveform for 3:8 Decoder

RTL Diagram for 8:1 Demultiplexer

Output Waveform for 8:1 Demultiplexer